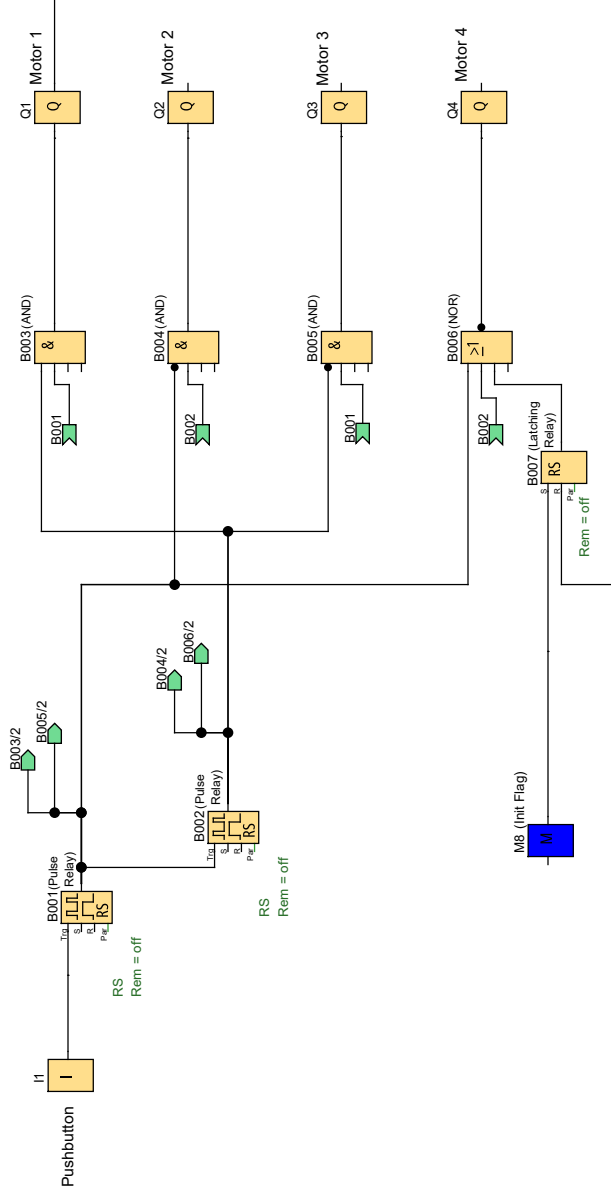


## Step control for 4 outputs



**A four-output step control system, initiated by a momentary pushbutton.**

The sequence progresses through two pulse relays, B001 and B002, which trigger outputs Q1, Q2, Q3 and Q4 through a series of AND and NOR gates, incorporating interlocks to prevent simultaneous activation.

**A latching relay (B007) is set by the Init Flag at startup & reset when Q1 is active.**

[illegible]



Connection	Label
I1	
M8	Init Flag
Q1	
Q2	
Q3	
Q4	

