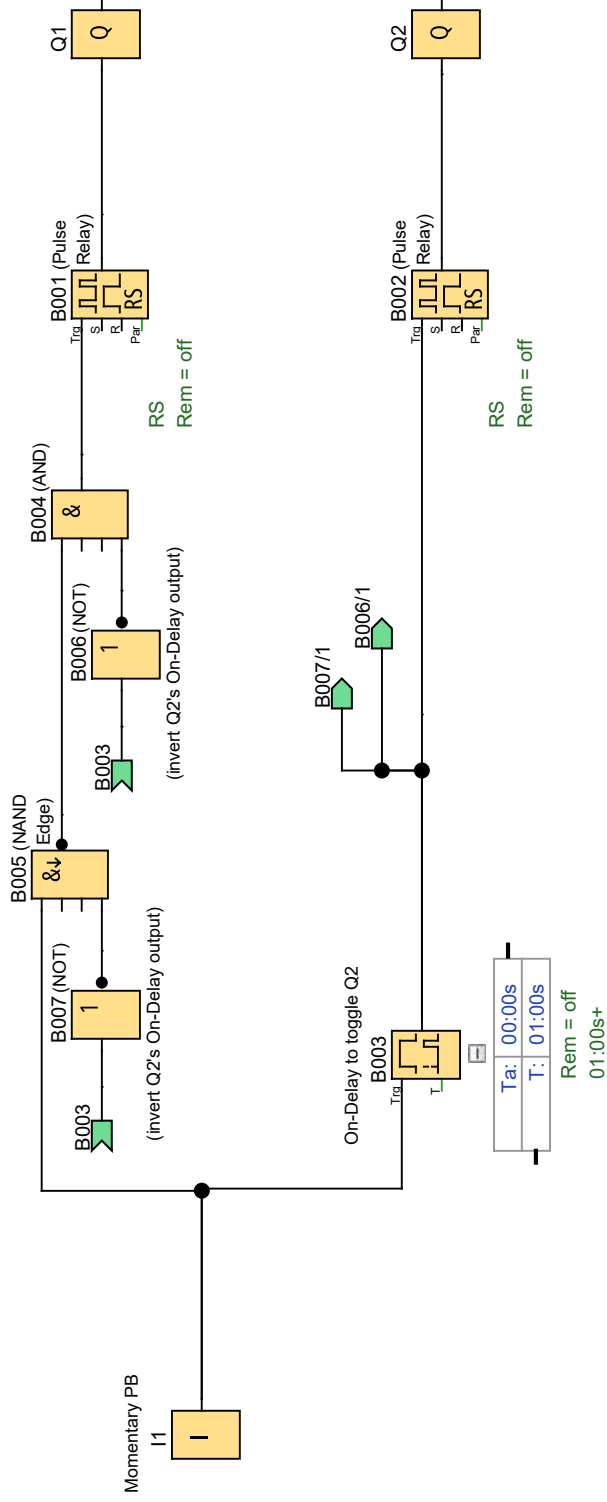


## Controlling two outputs with one momentary pushbutton

If Input 1 is pressed for a short moment, Q1 is toggled on/off.

If Input 1 is pressed for longer than 1 second, Q2 is toggled on/off.



Creator:		Project:	controlling two outputs with one pb FBD	Customer:	TWET Systems
Checked:		Installation:	Controlling 2 outputs with 1 pushbutton	Diagram No.:	
Date:	7/27/09 12:45 PM/7/29/25 2:05 PM	File:	controlling_two_outputs_with_one_pb_FBD.lsc	Page:	1 / 3

Block Number (Type)	Parameter
B001(Pulse Relay) : (Pulse Relay)	RS Rem = off
B002(Pulse Relay) : (Pulse Relay)	RS Rem = off
B003(On-Delay) : On-Delay to toggle Q2	Rem = off 01:00s+
B004(AND) : (AND)	
B005(NAND (Edge)) : (NAND Edge)	
B006(NOT) : (NOT)	
B007(NOT) : (NOT)	
I1(Input) : Momentary PB	

