

AND-Edge Gat

Q: what bit is controlling the output?

- Inputs 6 & 7, with Input 8 are required to energize Output3.

Switch Inputs 6, 7 & 8 to various positions and observe Output 3's counter behaviour. Complete the AND-Edge Gate Truth Table and identify the control bit

Q: what bit is controlling the output?

On=0+ Off=0

a3 (Da0.2)

0

2/B018

Q1 (DQ0.0)

OUTPUT CONTROL

0

Q2 (DQ0.1)

2/B005

NAND Gates:

- Inputs 1 & 2 are required to energize Output4.

Switch Inputs 1 & 2 to various positions and observe Output 4's counter behaviour. Complete the 2-input NAND Gate Truth Table and identify the control bit

Q: what bit is controlling the output?

Rem = off
On=0+
Off=0
Start=0

Rem = off
On=0+
Off=0

Q5 (DQ1.0)

0

2/B009

Q4 (DQ0.3)

0

2/B008

Q6 (DQ1.1)

2/B019

Rem = off
On=0+
Off=0
Start=0

Q7 (DQ1.2)

Disable unused outputs

0

Q8 (DQ1.3)


Inputs 3, 4 & 5 are required to energize Output5 (note the inverted NAND-block input).
 Switch Inputs 3, 4 & 5 to various positions and observe Output 5's behaviour.
 Complete the 3-input NAND Gate Truth Table and identify the control bit
 Q: what bit is controlling the output?


NAND-Edge Gate:


- Inputs 6 & 7, with Input 8 are required to energize Output6.

Switch Inputs 6, 7 & 8 to various positions and observe Output 6's counter behaviour. Complete the NAND-Edge Gate Truth Table and identify the control bit

Q: what bit is controlling the output?

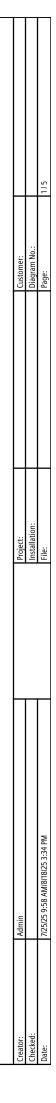

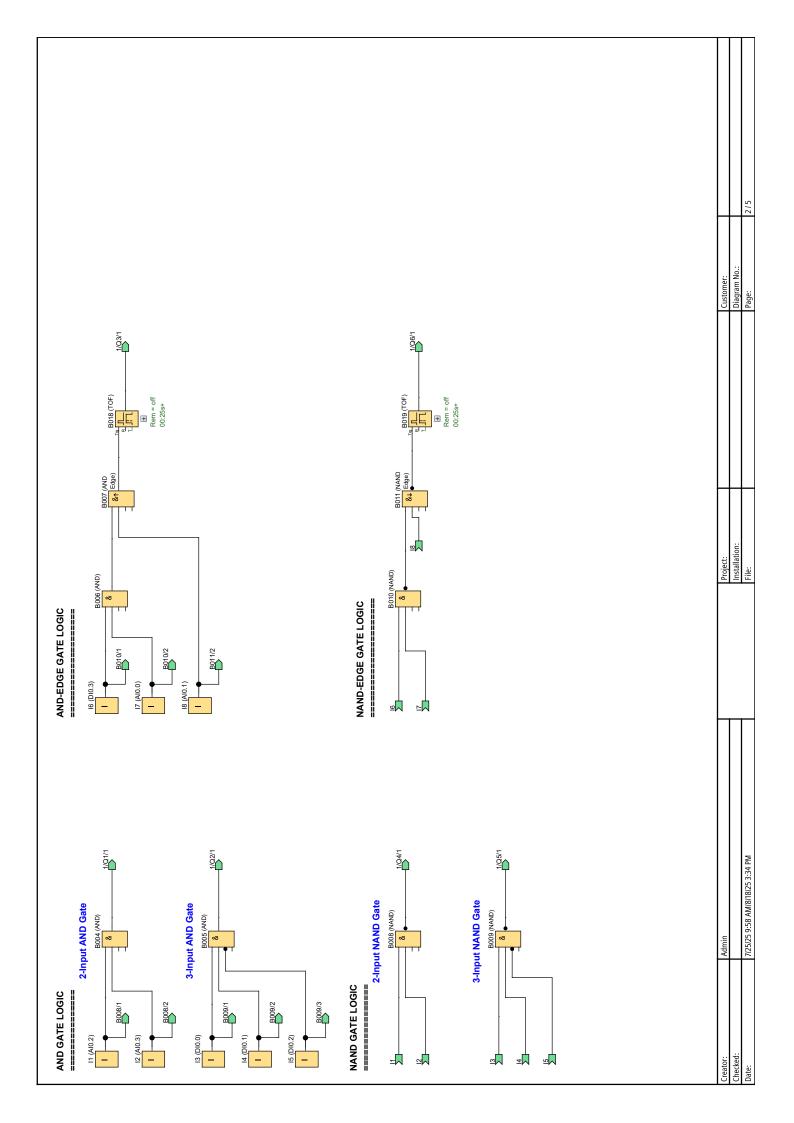

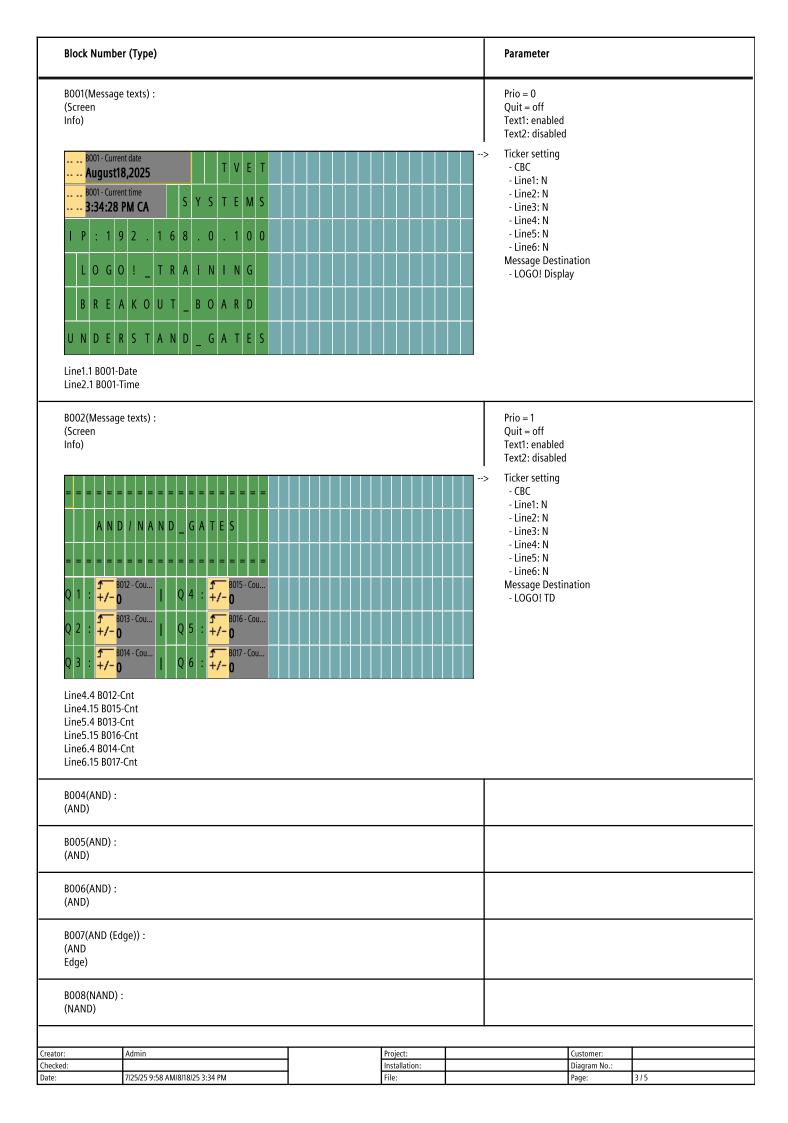

Block Number (Type)					Parameter				
BOO9(NAND): (NAND)									
B010(NAND): (NAND)									
B011(NAND (Edge)) : (NAND Edge)									
B012(Up/Down counter) : (Up/Dwn Counter)					Rem = off On=0+ Off=0 Start=0				
B013(Up/Down counter) : (Up/Dwn Counter)					Rem = off On=0+ Off=0 Start=0				
B014(Up/Dowr (Up/Dwn Counter)	B014(Up/Down counter) : (Up/Dwn Counter)					Rem = off On=0+ Off=0 Start=0			
B015(Up/Dowr (Up/Dwn Counter)	B015(Up/Down counter) : (Up/Dwn Counter)								
B016(Up/Dowr (Up/Dwn Counter)	B016(Up/Down counter) : (Up/Dwn Counter)					Rem = off On=0+ Off=0 Start=0			
B017(Up/Dowr (Up/Dwn Counter)	B017(Up/Down counter) : (Up/Dwn Counter)					Rem = off On=0+ Off=0 Start=0			
B018(Off-Dela (TOF)	B018(Off-Delay) : (TOF)					Rem = off 00:25s+			
B019(Off-Delag (TOF)	y):				Rem = off 00:25s+				
Crator	Admin		Droinet:			Cuctomor			
Checked:	Admin		Project: Installation:			Customer: Diagram No.:			
	7/25/25 9:58 AM/8/18/25 3:34 PM		File:			Page:	415		

Connection	Label
l1	AI0.2
12	AI0.3
13	DI0.0
14	DI0.1
15	DI0.2
16	DI0.3
17	AI0.0
18	AI0.1
M25	LOGO! displays white backlight
M26	LOGO! TD white backlight
Q1	DQ0.0
Q2	DQ0.1
Q3	DQ0.2
Q4	DQ0.3
Q5	DQ1.0
Q6	DQ1.1
Q7	DQ1.2
Q8	DQ1.3
X61	
X62	
X61	

Creator:	Admin	Project:	Customer:	
Checked:		Installation:	Diagram No.:	
Date:	7/25/25 9:58 AM/8/18/25 3:34 PM	File:	Page:	5/5